

HW III

32-bit Ripple Carry Adder Design

The simplest way to build an N-bit carry propagate adder is to chain together N full adders. The C_{out} of one stage acts as the C_{in} of the next stage, as shown in **Figure** below for 32-bit addition. This is called a ripple-carry adder. It is a good application of modularity and regularity: the full adder module is reused many times to form a larger system. The ripple-carry adder has the disadvantage of being slow when N is large. S_{31} depends on C_{30} , which depends on C_{29} , which depends on C_{28} , and so forth all the way back to C_{in} , as shown in blue in **Figure**. We say that the carry ripples through the carry chain. The delay of the adder, t_{ripple} , grows directly with the number of bits, given as $t_{ripple} = N * t_{FA}$ where t_{FA} is the delay of a full adder.

- Write VHDL code to design and simulate a 32-bit ripple carry adder with full adders. Do not instantiate all full adder by hand. Use another method.
- Suppose that we have 20ns delay for XOR gate and 15ns for and & or gates, then calculate overall delay for final result. Try to obtain the same result through simulation. Explain your results.

 


Figure. Ripple Carry Adder